



Cyprus
University of
Technology

EEN442 - Power Systems II (Συστήματα Ισχύος II)

Part 2: Fundamentals of power system operation

<https://sps.cut.ac.cy/courses/een442/>

Dr Petros Aristidou

Department of Electrical Engineering, Computer Engineering & Informatics

Last updated: March 17, 2025


After this part of the lecture and additional reading, you should be able to ...

- ① ... describe and analyse the behaviour of a transmission line under different operating conditions;
- ② ... explain the Ferranti effect;
- ③ ... use the PV and $P - \delta$ characteristics to determine the steady-state voltage and angle stability of a power system.

- In this part of the lecture, we investigate the stationary current and voltage relations as well as the resulting active and reactive power flows on an AC power line
- For this purpose, we use the wave equation discussed in EEN320
- Thereby, we focus on a series of practically relevant scenarios
- The analysis is performed under two assumptions:
 - 1) The operating conditions are balanced → analysis is performed via single-phase equivalent circuits
 - 2) The network is in steady-state (for assessment of dynamic phenomena other models are required)
- Furthermore, we consider all powers *per phase*. The corresponding three-phase power can be calculated using the conventions introduced in Part 1.

- 1 **Decoupled quantities**
- 2 **Surge impedance loading**
 - Surge impedance loading of a lossless power line
 - Surge impedance loading of a lossy power line
- 3 **The two extrema: No load and short circuit conditions**
 - No load conditions
 - Short circuit conditions
- 4 **Reactive power demand of a power line**
- 5 **Voltage drop across a power line**
- 6 **Efficiency of a high-voltage power line**
- 7 **Voltage-active power (P-V) characteristic of a high-voltage power line**
- 8 **Angle-active power (P- δ) characteristic of a high-voltage power line**

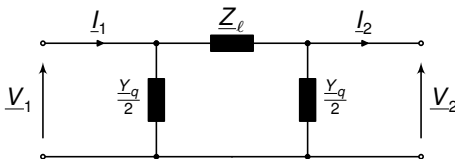- 1 **Decoupled quantities**
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power (P - V) characteristic of a high-voltage power line
- 8 Angle-active power (P - δ) characteristic of a high-voltage power line



where:


$$\underline{Z}_\ell = \underline{Z}_W \sinh(\underline{\gamma}\ell)$$

$$\frac{\underline{Y}_q}{2} = \frac{\cosh(\underline{\gamma}\ell) - 1}{\underline{Z}_W \sinh(\underline{\gamma}\ell)} = \frac{1}{\underline{Z}_W} \tanh\left(\frac{\underline{\gamma}\ell}{2}\right)$$

$$\underline{\gamma} = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

$$\underline{Z}_W = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

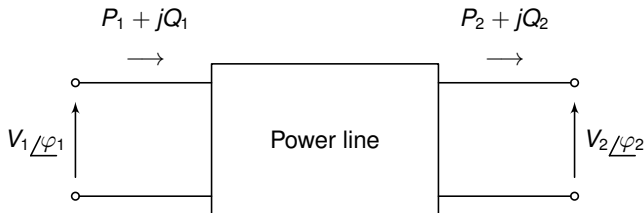
These parameters correspond to exact relations between currents and voltages according to wave equation for $x = 0$ and $x = \ell$




- Several ways to mathematically describe power flow over a power line
- Usually, we use complex voltage together with active and reactive powers at each end of line
- This yields 8 real quantities

$$V_1, \varphi_1, P_1, Q_1, V_2, \varphi_2, P_2, Q_2$$

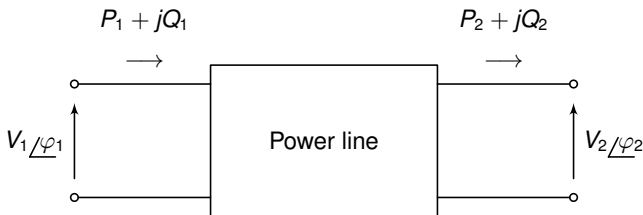- Which of the above quantities are decoupled (i.e. independent) of each other and which are not?




- Not all quantities in above graphic are independent of each other
- Examples:
 - \underline{V}_1 and \underline{V}_2 are coupled via line characteristics (see previous lectures)
 - Therefore it is customary to take one angle, e.g. φ_2 , as reference; hence, one "loses" one quantity in the formulas
 - Power flows are also coupled; if P_1 and Q_1 are fixed, then P_2 and Q_2 can be computed if \underline{V}_1 or \underline{V}_2 is fixed, too
 - If \underline{V}_1 and \underline{V}_2 are fixed, P_1 , P_2 , Q_1 and Q_2 are also fixed and can *not* be adjusted independently

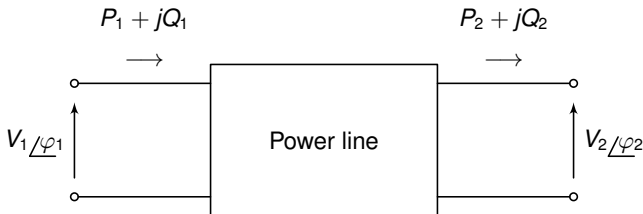

- V_1, φ_1, V_2 : powers result from line characteristics and given quantities; practical example: power line connects two bulk "stiff" power networks
- V_1, P_2, Q_2 (or P_1, Q_1, V_2): By fixing voltage on one end of line and power on other end, remaining quantities follow; practical example: consumer with fixed power demand connected via power line to network
- V_1, P_1, Q_1 : By fixing quantities at sending end of line, voltage and powers at receiving end follow; practical example: power plant that feeds network over power line

- 1 Decoupled quantities
- 2 **Surge impedance loading**
 - Surge impedance loading of a lossless power line
 - Surge impedance loading of a lossy power line
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power (P-V) characteristic of a high-voltage power line
- 8 Angle-active power (P- δ) characteristic of a high-voltage power line


2 Surge impedance loading - Meaning

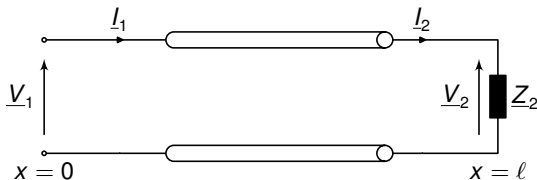

- Surge impedance loading (SIL) = power delivered when line is loaded with its surge impedance, i.e.

$$\underline{Z}_2 = \underline{Z}_w = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

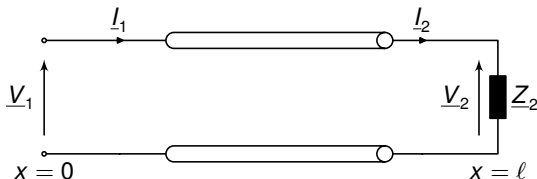- SIL also called natural loading
- In the following, we consider two cases
 - Lossless line ($R' = G' = 0$)
 - Lossy line ($R' \neq 0, G' \neq 0$)



- Lossless power line: $R' = G' = 0 \rightarrow$ surge impedance $Z_w = \sqrt{\frac{L'}{C'}}$

- Active power delivered at end of line

$$P_2 = \frac{|V_2|^2}{Z_2} = \frac{|V_2|^2}{Z_w}$$


- Reactive power delivered at end of line ($Z_2 = Z_w$ is real in lossless case)

$$Q_2 = 0$$

- Current at end of line

$$I_2 = \frac{V_2}{Z_2} = \frac{V_2}{Z_w}$$

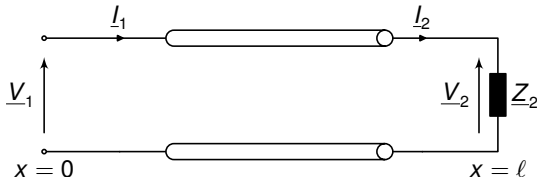2.1 SIL of lossless power line - Sending end (1)



- From full line model equations with $x = 0$ and $\underline{\gamma} = j\omega\sqrt{L'C'} = j\beta$

$$\underline{V}_1 = \cosh(j\beta\ell)\underline{V}_2 + Z_W \sinh(j\beta\ell)\underline{I}_2$$


$$\underline{I}_1 = \frac{\underline{V}_2}{Z_W} \sinh(j\beta\ell) + \cosh(j\beta\ell)\underline{I}_2$$

- With $\cosh(j\beta) = \cos(\beta)$ and $\sinh(j\beta) = j\sin(\beta)$ we obtain

$$\underline{V}_1 = \cos(\beta\ell)\underline{V}_2 + jZ_W \sin(\beta\ell)\underline{I}_2$$

$$\underline{I}_1 = j\frac{\underline{V}_2}{Z_W} \sin(\beta\ell) + \cos(\beta\ell)\underline{I}_2$$

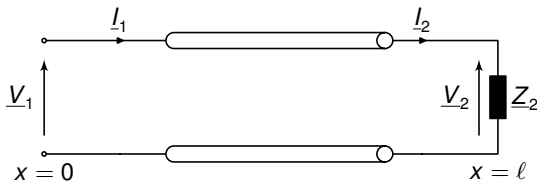
2.1 SIL of lossless power line - Sending end (2)



- Using $I_2 = \frac{V_2}{Z_w}$ yields

$$\begin{aligned}\underline{V}_1 &= \cos(\beta\ell)\underline{V}_2 + jZ_w \sin(\beta\ell)\frac{\underline{V}_2}{Z_w} \\ &= \underline{V}_2(\cos(\beta\ell) + j\sin(\beta\ell)) = \underline{V}_2 e^{j\beta\ell} \\ \underline{I}_1 &= j\frac{\underline{V}_2}{Z_w} \sin(\beta\ell) + \cos(\beta\ell)\frac{\underline{V}_2}{Z_w} \\ &= \underline{I}_2(\cos(\beta\ell) + j\sin(\beta\ell)) = \underline{I}_2 e^{j\beta\ell}\end{aligned}$$

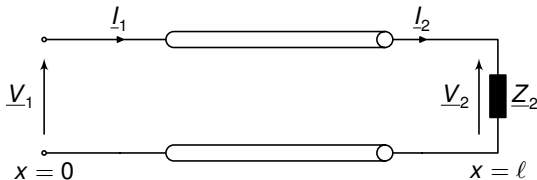→ Voltage and current are shifted by angle $\beta\ell$ at end of line
Thereby, their amplitudes remain unchanged




- For active power at both end of lines, we have that (as line is lossless)

$$P_1 = \underline{V}_1 \underline{I}_1^* = \underline{V}_2 \underline{I}_2^* = P_2 = \frac{|\underline{V}_1|^2}{Z_w}$$

- This particular loading of line is called *surge impedance loading (SIL)*

$$P_{SIL} = \frac{|\underline{V}|^2}{Z_w}$$

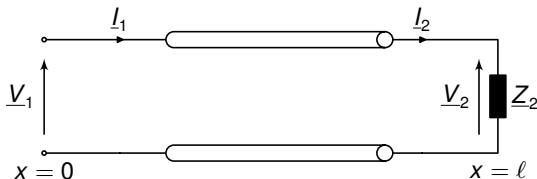- For this loading we achieve optimal transmission conditions (amplitudes of voltage and current remain constant along whole line)
- In practice, loading usually differs from SIL




- For SIL, *reactive power flow on line is zero*
- At each point on line, reactive power "absorption" of line inductance *equals* reactive power "production" of line capacitance

$$Q'_C = Q'_L \Rightarrow V^2 \omega C' = I^2 \omega L' \Rightarrow \frac{V^2}{I^2} = \frac{L'}{C'} = Z_w^2$$

- Surge impedance of overhead lines (OHLs) between 200 – 400 Ω
- OHL inductance significantly larger than OHL capacitance
- Reactive power "absorbed" by OHL inductance exceeds reactive power "produced" by OHL capacitance even for small currents
- OHLs often operated above their SIL; then they "absorb" reactive power
 - Compared to OHLs, cables have very low surge impedance ($\approx 30 - 50 \Omega$)
- SIL usually above thermal limit of cable
- Cables usually "produce" reactive power

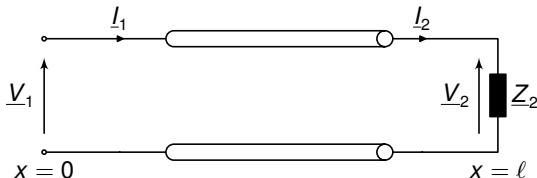2.2 SIL of lossy power line - Sending end (1)




- Lossy line $\rightarrow \underline{Z}_w$ is complex
- As before, we consider the case $\underline{Z}_2 = \underline{Z}_w$
- Current at receiving end of line

$$\underline{I}_2 = \frac{\underline{V}_2}{\underline{Z}_2} = \frac{\underline{V}_2}{\underline{Z}_w}$$

- Apparent power at receiving end of line

$$\underline{S}_2 = P_2 + jQ_2 = \underline{V}_2 \underline{I}_2^* = \frac{|\underline{V}_2|^2}{\underline{Z}_w^*}$$

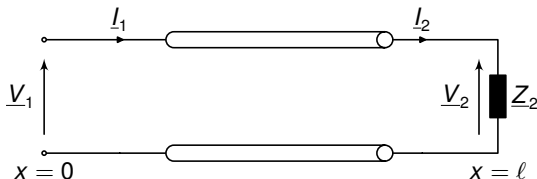


- From solution of wave equation with $x = 0$ and $\underline{\gamma} = \alpha + j\beta$ (see EEN320, transmission line characteristics)

$$\begin{aligned}
 \underline{V}_1 &= \cosh(\underline{\gamma}\ell)\underline{V}_2 + \underline{Z}_w \sinh(\underline{\gamma}\ell)\underline{I}_2 \\
 &= \cosh(\underline{\gamma}\ell)\underline{V}_2 + \underline{Z}_w \sinh(\underline{\gamma}\ell)\frac{\underline{V}_2}{\underline{Z}_w} \\
 &= \underline{V}_2 (\cosh(\underline{\gamma}\ell) + \sinh(\underline{\gamma}\ell)) = \underline{V}_2 e^{\underline{\gamma}\ell} \\
 \underline{I}_1 &= \frac{\underline{V}_2}{\underline{Z}_w} \sinh(\underline{\gamma}\ell) + \cosh(\underline{\gamma}\ell)\underline{I}_2 \\
 &= \underline{I}_2 (\cosh(\underline{\gamma}\ell) + \sinh(\underline{\gamma}\ell)) = \underline{I}_2 e^{\underline{\gamma}\ell}
 \end{aligned}$$

Note: To obtain the last equality, we have used $\cosh(x) + \sinh(x) = e^x$

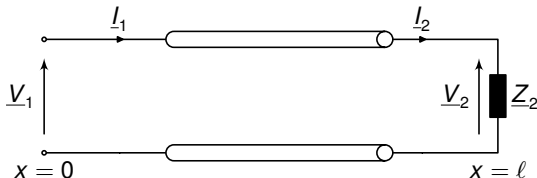2.2 SIL of lossy power line - Sending end (3)



- Apparent power at sending end

$$\underline{S}_1 = P_1 + jQ_1 = \underline{V}_1 \underline{I}_1^* = \underline{V}_2 \frac{\underline{V}_2^*}{\underline{Z}_w^*} e^{2\alpha \ell} = \underline{S}_2 e^{2\alpha \ell}$$

- As in lossless case, phase angle between voltage and current remains constant along line; phase shift is proportional to βx
- But now, active and reactive power decrease with line length; same applies to voltage and current

Table: Typical values for OHLs¹

Rated voltage in kV	132	275	400
\underline{Z}_w [Ω]	373	302	296
P_{SIL} [MW]	47	250	540

Table: Typical values for cables²

Rated voltage in kV	115	230	500
\underline{Z}_w [Ω]	36.2	37.1	50.4
P_{SIL} [MW]	365	1426	4960


¹ Source: B. M. Weedy et al., "Electric Power Systems", John Wiley & Sons, 2012

² Source: P. Kundur, "Power System Stability", McGraw-Hill, 1994


- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 **The two extrema: No load and short circuit conditions**
 - No load conditions
 - Short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power (P-V) characteristic of a high-voltage power line
- 8 Angle-active power (P- δ) characteristic of a high-voltage power line

- Next, we analyse the behaviour of a power line in two special cases
 - No load
 - Short circuit
- To simplify our calculations, we restrict ourselves to the lossless case

3.1 No load conditions - Setup

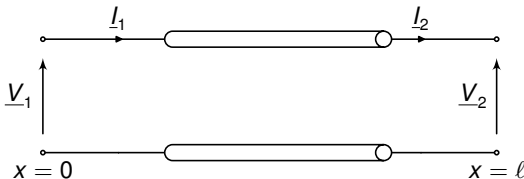

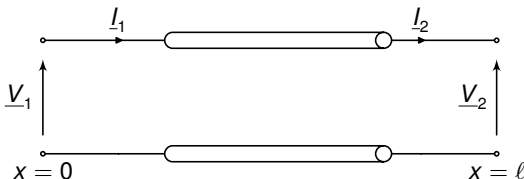- No load condition can occur if
 - Voltage is applied to unloaded line
 - Load at end of line is disconnected
- Main characteristic: $\underline{I}_2 = 0$



- Solution of wave equation with $x = 0$ and $\underline{\gamma} = j\omega\sqrt{L'C'} = j\beta$ yields (see Part 5, Sect. 4.2)


$$\underline{V}_1 = \cos(\beta\ell)\underline{V}_2$$

$$\underline{I}_1 = j\frac{\underline{V}_2}{Z_W} \sin(\beta\ell)$$

- Recall that we may fix one of two voltage angles. Setting $\varphi_1 = 0$, we have

$$V_1 = \cos(\beta\ell)V_2$$
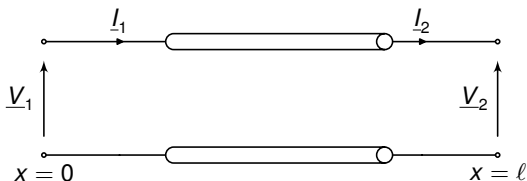
$$I_1 = j\frac{V_2}{Z_W} \sin(\beta\ell)$$







- Keeping V_1 constant, we get

$$V_2 = \frac{V_1}{\cos(\beta\ell)}$$
$$I_1 = \frac{jV_2}{Z_w} \sin(\beta\ell) = \frac{jV_1 \tan(\beta\ell)}{Z_w}$$

- Voltage amplitude increases along line, while that of current decreases ($I_2 = 0$)
- This phenomenon is called *Ferranti effect* (because it was first observed by the British engineer Sebastian Ziani de Ferranti in 1887)

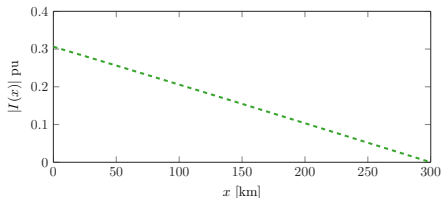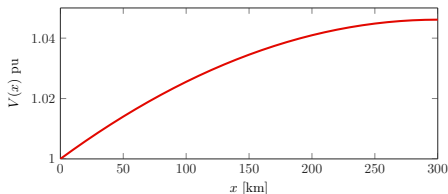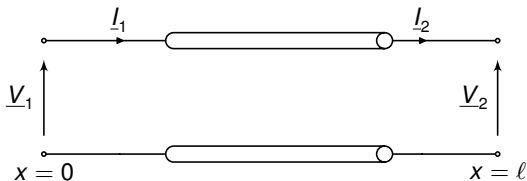3.1 No load conditions - Ferranti effect illustration



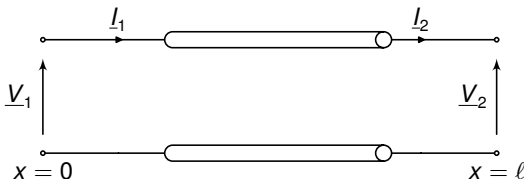

- It holds that (ϵ_0 is electric constant and μ_0 magnetic constant)


$$\beta = \omega \sqrt{L' C'} \approx \omega \sqrt{\epsilon \epsilon_0 \mu_0}$$

- Permittivity of air $\epsilon = 1$
- For $\omega = 2\pi 50$ [rad/s], we have that $\beta \approx \frac{6^\circ}{100 \text{ km}}$

→ Extreme scenario: resonance; achieved for 50 Hz at $\ell = 1500 \text{ km}$

$$\beta \ell = \frac{6^\circ \times 1500 \text{ km}}{100 \text{ km}} = 90^\circ = \frac{\pi}{2}$$

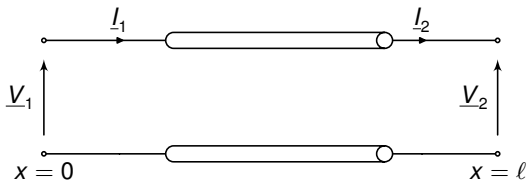- Then $\cos(\beta \ell) = 0$ and $V_2 \rightarrow \infty$



- Impedance at sending end


$$\underline{Z}_1 = \frac{\underline{V}_1}{\underline{I}_1} = -j \frac{Z_w}{\tan(\beta \ell)}$$

- We can see that impedance has *capacitive* character

→ High loading currents required!

- In practice: amplitude of \underline{V}_1 not stiff, but additionally increased by loading currents → need to be careful with voltage rise already for line lengths of 300km

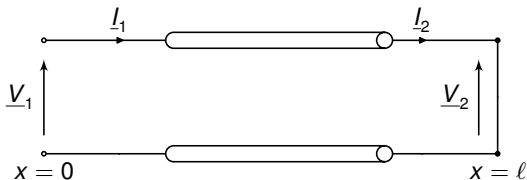3.2 Short circuit conditions - Voltage and current



- Short circuit $\rightarrow \underline{V}_2 = 0$
- Solution of wave equation with $x = 0$ and $\underline{\gamma} = j\omega\sqrt{L'C'} = j\beta$ yields (see EEN320 for more details)


$$\underline{V}_1 = j\underline{I}_2 Z_w \sin(\beta\ell)$$

$$\underline{I}_1 = \underline{I}_2 \cos(\beta\ell)$$

- In analogy to voltage in no load condition, now current increases along line

$$\underline{I}_2 = \frac{\underline{I}_1}{\cos(\beta\ell)}$$

3.2 Short circuit conditions - Impedance

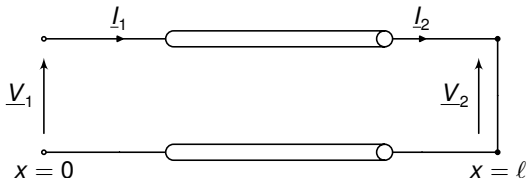


- Short circuit impedance


$$\frac{\underline{V}_1}{\underline{I}_1} = \underline{Z}_1 = jZ_w \tan(\beta\ell)$$

- For $\omega = 2\pi 50$ [rad/s], short circuit impedance is *inductive* for line lengths < 1500 km
- As before, resonance $|\underline{I}_2| \rightarrow \infty$ for $\beta\ell = \pi/2$

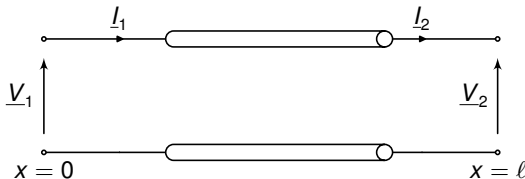- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line**
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power ($P-V$) characteristic of a high-voltage power line
- 8 Angle-active power ($P-\delta$) characteristic of a high-voltage power line




- Power transmission over a power line causes losses:
 - Ohmic components of line (resistance; conductance) cause active power losses
 - Reactive components of line (inductance; capacitance) influence reactive power flow
- Apparent power at receiving end of line differs from apparent power at sending end!
- For voltage relation along line, reactive power is most important as discussed hereafter for *lossless* line

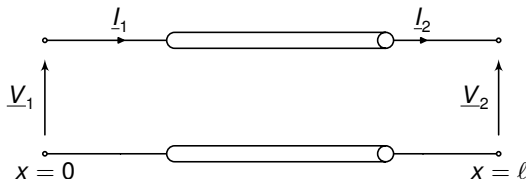

- Wave equation for *lossless* line

$$\begin{bmatrix} \underline{V}_1 \\ \underline{I}_1 \end{bmatrix} = \begin{bmatrix} \cos(\beta\ell) & jZ_w \sin(\beta\ell) \\ j\frac{\sin(\beta\ell)}{Z_w} & \cos(\beta\ell) \end{bmatrix} \begin{bmatrix} \underline{V}_2 \\ \underline{I}_2 \end{bmatrix}$$

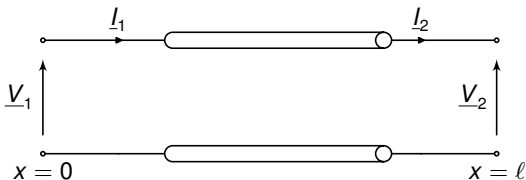→ Apparent power $\underline{S}_1 = \underline{V}_1 \underline{I}_1^* = P_1 + jQ_1$ at sending end is dependent on
apparent power $\underline{S}_2 = \underline{V}_2 \underline{I}_2^* = P_2 + jQ_2$ at receiving end of line



- Hence, we have

$$\underline{S}_1 = \underline{V}_1 \underline{I}_1^* = P_1 + jQ_1 = j \cos(\beta \ell) \sin(\beta \ell) \left(|\underline{I}_2|^2 - |\underline{V}_2|^2 \frac{1}{Z_w} \right) + \sin^2(\beta \ell) \underline{I}_2 \underline{V}_2^* + \cos^2(\beta \ell) \underline{V}_2 \underline{I}_2^*$$

- For our analysis, it is convenient to fix \underline{V}_2 and express \underline{S}_1 in terms of SIL

$$P_{SIL} = \frac{|\underline{V}_2|^2}{Z_w}$$

- Using the relations

$$|\underline{V}_2|^2 = P_{SIL} Z_w$$

$$\underline{I}_2^* = \frac{\underline{S}_2}{\underline{V}_2} \rightarrow |\underline{I}_2|^2 = \frac{|\underline{S}_2|^2}{|\underline{V}_2|^2} = \frac{|\underline{S}_2|^2}{P_{SIL} Z_w}$$

$$\underline{I}_2 \underline{V}_2^* = (\underline{V}_2 \underline{I}_2^*)^* = \underline{S}_2^* = P_2 - jQ_2$$

$$\cos^2(\beta\ell) - \sin^2(\beta\ell) = \cos(2\beta\ell)$$

$$\cos(\beta\ell) \sin(\beta\ell) = \frac{1}{2} \sin(2\beta\ell)$$

we can rewrite the equation for \underline{S}_1 as follows

$$\underline{S}_1 = P_1 + jQ_1 = P_2 + j \left(Q_2 \cos(2\beta\ell) + \frac{1}{2} \sin(2\beta\ell) \left(\frac{|\underline{S}_2|^2}{P_{SIL}} - P_{SIL} \right) \right)$$

- For lossless line

$$P_1 = P_2 \rightarrow \text{can focus further analysis on reactive power flows}$$

- Relation of reactive power flows

$$Q_1 = Q_2 \cos(2\beta\ell) + \frac{1}{2} \sin(2\beta\ell) \left(\frac{|\underline{S}_2|^2}{P_{SIL}} - P_{SIL} \right)$$


- Q_1 dependent on Q_2 ("load demand") and reactive power demand of line
- With simplifying approximation $\cos(2\beta\ell) \approx 1$, reactive power demand of line given by

$$\Delta Q = Q_1 - Q_2 \approx \underbrace{\frac{1}{2} \sin(2\beta\ell) \frac{|\underline{S}_2|^2}{P_{SIL}}}_{\text{inductive component } Q_L} - \underbrace{\frac{1}{2} \sin(2\beta\ell) P_{SIL}}_{\text{capacitive component } Q_C}$$

- $|\underline{S}_2| = P_{SIL} \rightarrow \Delta Q = 0$
- $|\underline{S}_2| = 0 \rightarrow \Delta Q < 0$ line produces reactive power ($Q_L = 0$, $Q_C > 0$)
- $|\underline{S}_2| > P_{SIL} \rightarrow \Delta Q > 0$ line absorbs reactive power ($Q_L > Q_C$)
- $|\underline{S}_2| < P_{SIL} \rightarrow \Delta Q < 0$ line produces reactive power ($Q_L < Q_C$)


- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line**
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power (P - V) characteristic of a high-voltage power line
- 8 Angle-active power (P - δ) characteristic of a high-voltage power line

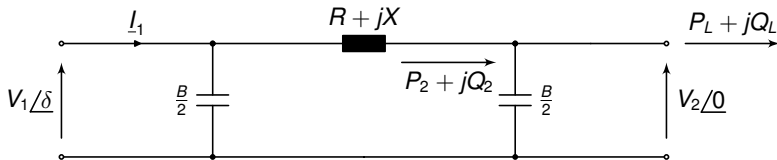5 Voltage drop across a power line - Setup



- Π -model of power line of length ℓ and $G' = 0$, $R = R'\ell$, $X = \omega L'\ell$ and $B = \omega C'\ell$
- Load at end of line: $P_L + jQ_L$
- We want to derive a formula for voltage drop across line
- For this purpose it is convenient to define V_2 on real line and denote angle between V_2 and \underline{V}_1 by δ

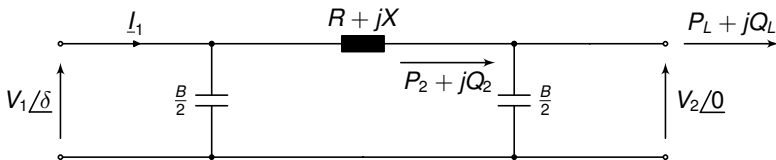5 Voltage drop across a power line - A simplification (1)




- Shunt elements B produce reactive power
- We can obtain "net" reactive power flow Q_2 on line by subtracting reactive power Q_C produced by B from Q_L , i.e.,


$$P_2 = P_L$$

$$Q_2 = Q_L - Q_C$$

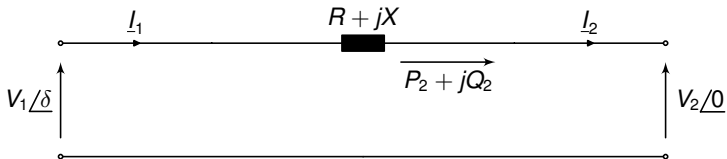5 Voltage drop across a power line - A simplification (2)



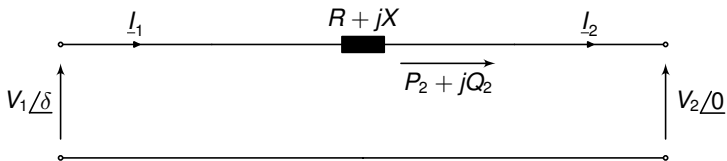- By using $Q_2 = Q_L - Q_C$ we can simplify considered circuit as shown above



- Current I_2 as function of apparent power $\underline{S}_2 = P_2 + jQ_2$ and $\underline{V}_2 = V_2$



$$I_1 = I_2 = \frac{\underline{S}_2^*}{\underline{V}_2} = \frac{P_2 - jQ_2}{V_2}$$

- Voltage \underline{V}_1


$$\begin{aligned}\underline{V}_1 &= V_2 + (R + jX)I_2 = V_2 + (R + jX)\frac{P_2 - jQ_2}{V_2} \\ &= \left(V_2 + \frac{RP_2 + XQ_2}{V_2}\right) + j\left(\frac{XP_2 - RQ_2}{V_2}\right)\end{aligned}$$

$$|\underline{V}_1| = V_1 = \sqrt{\left(V_2 + \frac{RP_2 + XQ_2}{V_2}\right)^2 + \left(\frac{XP_2 - RQ_2}{V_2}\right)^2}$$

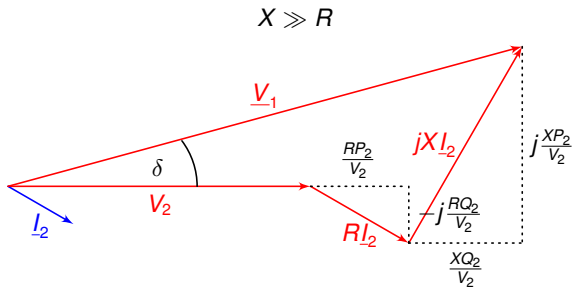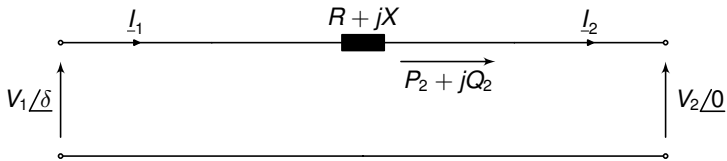5 Voltage drop across a power line - Phasor diagram



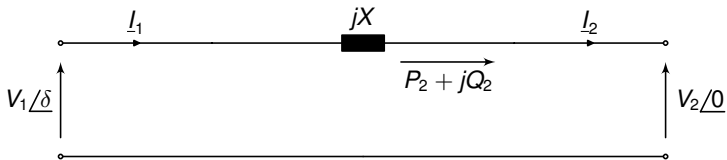5 Voltage drop across a power line - Lossless line



- Lossless line $\rightarrow R = 0$
- Expression for V_1 simplifies to


$$\underline{V}_1 = V_1 \cos(\delta) + jV_1 \sin(\delta) = \left(V_2 + \frac{XQ_2}{V_2} \right) + j \left(\frac{XP_2}{V_2} \right)$$

- Separating the real with the imaginary parts, gives

$$P_2 = \frac{V_1 V_2 \sin(\delta)}{X}$$

$$Q_2 = \frac{V_1 V_2 \cos(\delta) - V_2^2}{X}$$

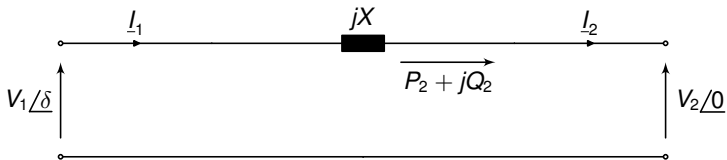5 Voltage drop across a power line - Lossless line



- The magnitude of V_1 is given by


$$|\underline{V}_1| = V_1 = \sqrt{\left(V_2 + \frac{XQ_2}{V_2}\right)^2 + \left(\frac{XP_2}{V_2}\right)^2}$$

- In most scenarios $|XP_2/V_2| \ll V_2$ and expression for V_1 can be further simplified to

$$|\underline{V}_1| = V_1 \approx V_2 + \frac{XQ_2}{V_2}$$


→ $\Delta V = V_1 - V_2$ mainly influenced by reactive power Q_2 !

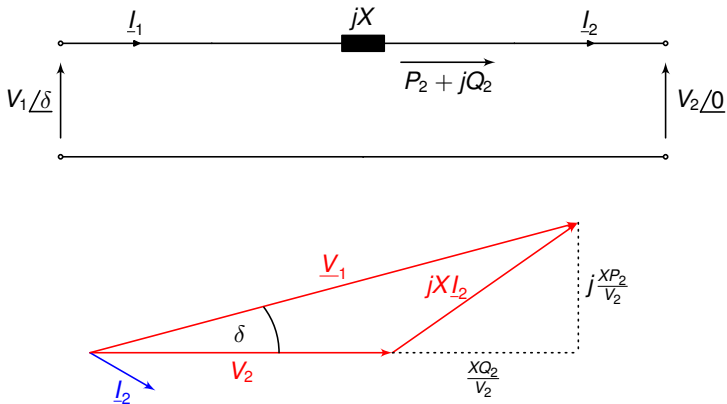5 Voltage drop across a power line - Lossless line phasor diagram



→ Phase angle δ mainly influenced by active power P_2 !

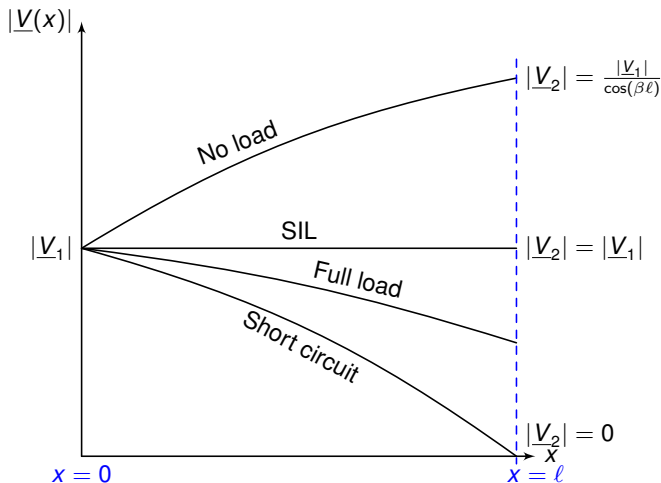
- We have assumed \underline{V}_2 and \underline{S}_2 are known and we want to calculate \underline{V}_1 ; often also V_1 and \underline{S}_2 given and we seek to compute \underline{V}_2 ; this can be done in an equivalent manner



- The discussed scenarios mainly apply to OHLs; cables typically have different properties

- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line**
- 7 Voltage-active power (P - V) characteristic of a high-voltage power line
- 8 Angle-active power (P - δ) characteristic of a high-voltage power line

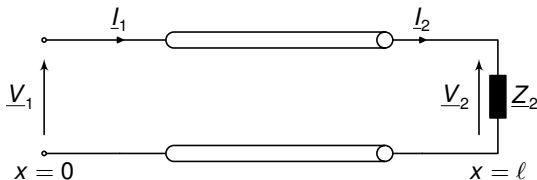6 Efficiency of a high-voltage power line - An example (1)




- Consider exemplary 200 km/420 kV ($= V_{LL} = \sqrt{3}V_2$) power line with following characteristics

$$R' = 0.031 \, \Omega/\text{km}, \quad L' = 1.06 \, \text{mH}/\text{km}, \quad C' = 11.9 \, \text{nF}/\text{km}, \quad G' = 0, \quad f = 50 \, \text{Hz}$$

- Assume line is loaded with surge impedance $\underline{Z}_2 = \underline{Z}_w$
- Propagation constant

$$\underline{\gamma} = \sqrt{(0.031 + j0.333)j3.74 \cdot 10^{-6}} = (0.052 + j1.117)10^{-3}$$
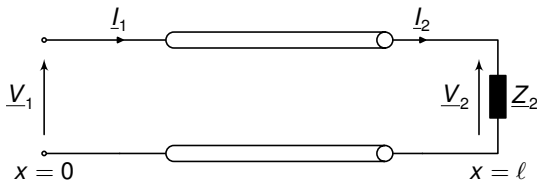
$$\underline{\gamma}\ell = \alpha\ell + j\beta\ell = 0.0104 + j0.2234$$



- Characteristic impedance (neglecting imaginary part)


$$Z_w = 298.5 \, \Omega$$

- Active power drawn by load at receiving end of line

$$P_2 = \frac{V_{LL}^2}{Z_w} \approx 591 \, \text{MW}$$

- Current RMS magnitude (per phase)
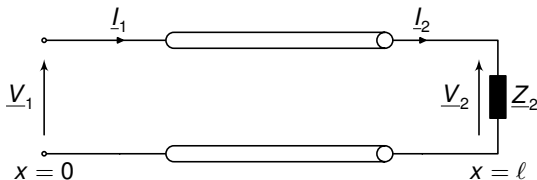
$$I_2 = \frac{\frac{V_{LL}}{\sqrt{3}}}{Z_w} = \frac{420 \, \text{kV}}{\sqrt{3} \cdot 298.5 \, \Omega} = 812.4 \, \text{A}$$



- Line losses can be approximated by

$$\Delta P = P_1 - P_2 \approx 3R'\ell I_2^2 = 3 \cdot 0.031 \cdot 200 \cdot 812.4^2 = 12.3 \text{ MW}$$


- $P_1 = P_2 + \Delta P \approx 591 + 12.3 = 603.3 \text{ MW}$
- Alternative:** We can calculate exact value for P_1 from wave equation (see Part 6 Section 2.2)

$$P_1 = P_2 e^{2\alpha\ell} = 603.6 \text{ MW}$$


- Our approximation is fairly accurate
- Very high efficiency for power transmission!

$$e^{-2\alpha\ell} = 0.979 \quad \leftrightarrow \quad 97.9\%$$

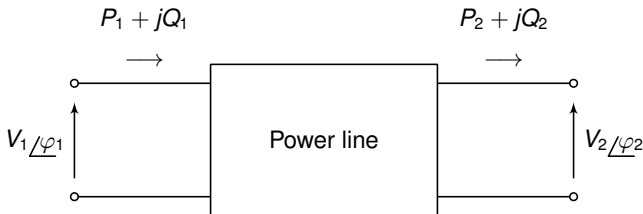- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power ($P-V$) characteristic of a high-voltage power line**
- 8 Angle-active power ($P-\delta$) characteristic of a high-voltage power line



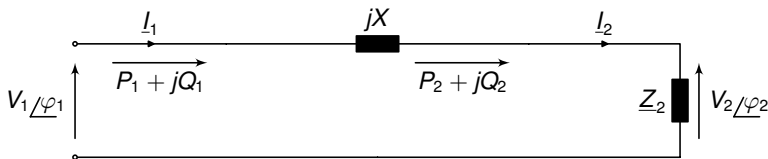- We have seen that power flows over a line affect voltages at sending and receiving end
- If load demand at receiving end is too large, then voltage drop can be significant and even lead to *voltage instability*
- Therefore, it is important to understand relation between voltage drop and load demand




- Suppose that $V_1 = 1$ pu, $\varphi_1 = 0$ and that power line is lossless
 $R' = G' = 0$
- We have that $\underline{I}_1 = \underline{I}_2$,

$$\underline{V}_2 = \underline{V}_1 - jX\underline{I}$$

and with $\delta = \varphi_1 - \varphi_2 = -\varphi_2$
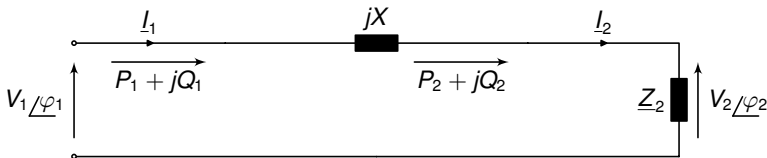
$$\begin{aligned} \underline{S}_2 &= \underline{V}_2 \underline{I}^* = \underline{V}_2 \frac{\underline{V}_1 - \underline{V}_2^*}{-jX} \\ &= \frac{j}{X} \left(V_1 V_2 \cos(\delta) + jV_1 V_2 \sin(\delta) - V_2^2 \right) \end{aligned}$$




- Decomposing \underline{S}_2 in real and imaginary parts yields

$$P_2 = -\frac{V_1 V_2}{X} \sin(\delta)$$

$$Q_2 = \frac{1}{X} (V_1 V_2 \cos(\delta) - V_2^2)$$

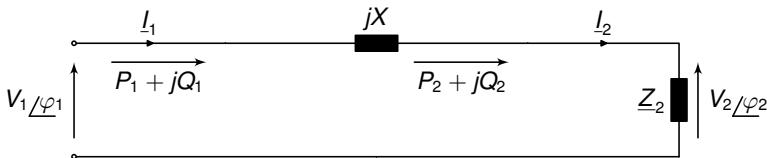7 P-V characteristic - Active and reactive power flow sending end



- Same procedure as for receiving end

$$\underline{S}_1 = \underline{V}_1 \underline{I}^* = \underline{V}_1 \frac{\underline{V}_1 - \underline{V}_2^*}{-jX}$$

- Decomposing \underline{S}_1 in real and imaginary parts yields

$$P_1 = \frac{V_1 V_2}{X} \sin(\delta)$$

$$Q_1 = \frac{1}{X} \left(V_1^2 - V_1 V_2 \cos(\delta) \right)$$

- These equations are called *power flow* or *load flow* equations of the lossless system

- When does a solution to power flow equations exist?

$$X^2 P_2^2 = (V_1 V_2 \sin(\delta))^2$$

$$(XQ_2 + V_2^2)^2 = (V_1 V_2 \cos(\delta))^2$$

$$\Rightarrow 0 = (V_2^2)^2 + (2Q_2X - V_1^2)V_2^2 + X^2(P_2^2 + Q_2^2)$$

- The above is a quadratic equation in $y = V_2^2$, i.e.,

$$cy^2 + by + a = 0 \quad c = 1 \quad b = (2Q_2X - V_1^2) \quad a = X^2(P_2^2 + Q_2^2)$$

- Condition for existence of at least one real solution (see quadratic formula)

$$b^2 - 4ac \geq 0$$

$$\Leftrightarrow (2Q_2X - V_1^2)^2 - 4X^2(P_2^2 + Q_2^2) = V_1^4 - 4X^2P_2^2 - 4Q_2XV_1^2 \geq 0$$

- Solution to quadratic equation


$$y_{1,2} = \frac{V_1^2}{2} - Q_2 X \pm \sqrt{\frac{V_1^4}{4} - X^2 P_2^2 - X Q_2 V_1^2}$$

- Voltage magnitude at receiving end

$$V_2 = \sqrt{y_{1,2}} = \sqrt{\frac{V_1^2}{2} - Q_2 X \pm \sqrt{\frac{V_1^4}{4} - X^2 P_2^2 - X Q_2 V_1^2}}$$

- To each loading $\underline{S}_2 = P_2 + jQ_2$ there exist, in general, two real solutions for V_2 !

7 P-V characteristic - $P - V$ curve

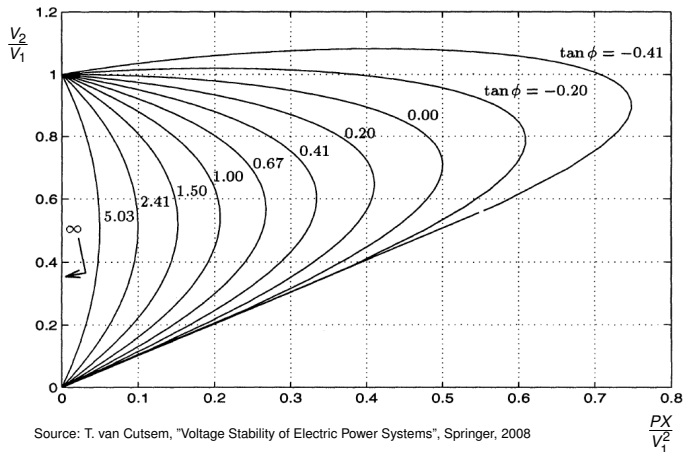


- Due to its shape, $P - V$ curve is also called *nose curve*
- Power factor: $\cos(\phi) = \frac{P}{|S|} \rightarrow Q = P \tan(\phi)$


- Power transfer is limited by power factor
 - Power factor has significant influence on voltage magnitude at receiving end of line
 - Inductive load ($\tan(\varphi) > 0$): lower transmittible active power and lower voltage magnitude V_2
 - Capacitive load ($\tan(\varphi) < 0$): higher transmittible active power and flatter voltage profile in upper part of nose curve
- Voltage V_2 can be regulated ("parallel compensation") with additional capacitances (compare Part 2 of lecture)
- Specific active power value can be achieved at two different voltage magnitudes
 - Usually, higher value chosen (≈ 1 pu) as results in lower current and also low voltage values can lead to instability

- Power transfer is limited by power factor
 - Power factor has significant influence on voltage magnitude at receiving end of line
 - Inductive load ($\cos(\varphi)$ ind.): lower transmittable active power and lower voltage magnitude V_2
 - Capacitive load ($\cos(\varphi)$ cap.): higher transmittable active power and flatter voltage profile in upper part of nose curve
- Voltage V_2 can be regulated ("parallel compensation") with additional capacitances (compare Part 2 of lecture)
- Specific active power value can be achieved at two different voltage magnitudes
 - Usually, higher value chosen (≈ 1 pu) as results in lower current and also low voltage values can lead to instability

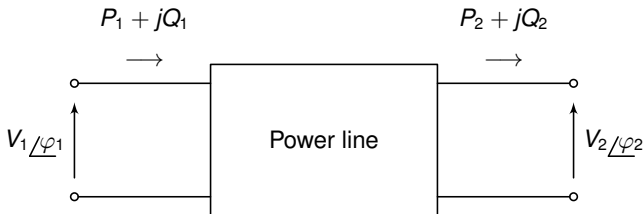- 1 Decoupled quantities
- 2 Surge impedance loading
- 3 The two extrema: No load and short circuit conditions
- 4 Reactive power demand of a power line
- 5 Voltage drop across a power line
- 6 Efficiency of a high-voltage power line
- 7 Voltage-active power (P - V) characteristic of a high-voltage power line
- 8 Angle-active power (P - δ) characteristic of a high-voltage power line**



- Another important relation is that between the transmitted active power flow and the phase angle difference between the voltages at sending and receiving end of line (i.e., $\underline{V}_1 = V_1/\varphi_1$ and $\underline{V}_2 = V_2/\varphi_2$)
- We conduct our analysis under the following assumptions
 - The voltage magnitudes V_1 and V_2 are constant
 - The line impedance is purely inductive, i.e., $\underline{Z}_\ell = jX = j\omega L'\ell$
- However, the phase angle difference $\delta = \varphi_1 - \varphi_2$ may vary

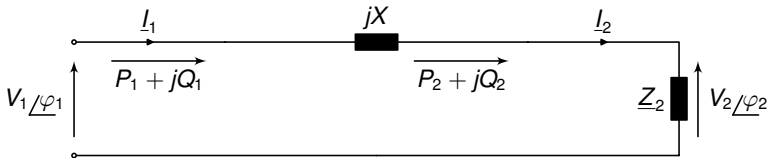


- Voltages in polar form

$$\underline{V}_1 = V_1 e^{j\varphi_1} \quad \underline{V}_2 = V_2 e^{j\varphi_2}$$

- Lossless line $\rightarrow P_1 = P_2 = \Re(\underline{V}_1 \underline{I}_1^*)$


$$\underline{I}_1 = \underline{I}_2 = \frac{\underline{V}_1 - \underline{V}_2}{jX} = \frac{V_1 e^{j\varphi_1} - V_2 e^{j\varphi_2}}{jX}$$
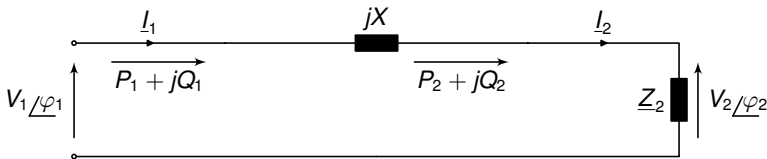
$$\underline{I}_1^* = \frac{V_1 e^{-j\varphi_1} - V_2 e^{-j\varphi_2}}{-jX}$$



- Without loss of generality, we set $\varphi_2 = 0$
- Then with *transmission angle* $\delta = \varphi_1 - \varphi_2$

$$\begin{aligned}
 P = P_1 = P_2 &= \Re \left(V_1 e^{j\varphi_1} \frac{j}{X} \left(V_1 e^{-j\varphi_1} - V_2 \right) \right) = \Re \left(jV_1^2 \frac{1}{X} - j\frac{1}{X} V_1 V_2 e^{j\varphi_1} \right) \\
 &= \Re \left(jV_1^2 \frac{1}{X} - jV_1 V_2 \frac{1}{X} \cos(\varphi_1) + V_1 V_2 \frac{1}{X} \sin(\varphi_1) \right) \\
 &= V_1 V_2 \frac{1}{X} \sin(\varphi_1) = V_1 V_2 \frac{1}{X} \sin(\delta)
 \end{aligned}$$

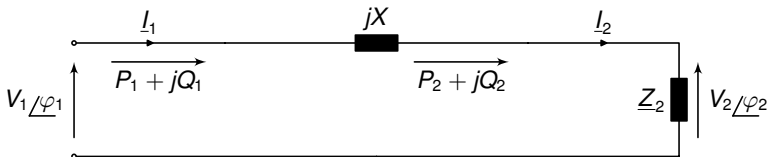

- We can rewrite active power in terms of characteristic impedance Z_w , phase constant β and line length ℓ (see Part 5 Section 4.4)


$$P = P_1 = P_2 = V_1 V_2 \frac{1}{X} \sin(\delta) = V_1 V_2 \frac{\sin(\delta)}{Z_w \sin(\beta \ell)} \quad P_{SIL} = \frac{|V_B|^2}{Z_w}$$

$$\rightarrow \frac{P}{P_{SIL}} = v_1 v_2 \frac{\sin(\delta)}{\sin(\beta \ell)}$$

- Example: $\ell = 400$ km, $\beta \ell = 0.52$ rad, $v_1 = v_2 = 1$ pu

$$P_{\max} = \frac{1}{\sin(\beta \ell)} = 2.012 P_{SIL}$$

8 P- δ characteristic - Diagram

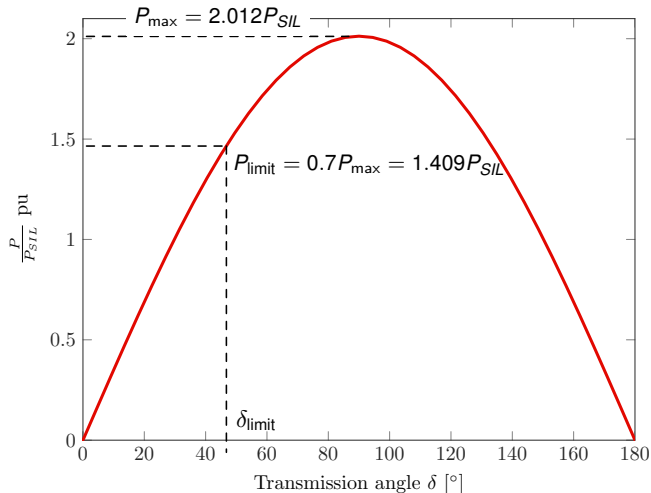

● $\delta_{\text{limit}} \approx 40^\circ$

- Power lines can not be loaded arbitrarily heavily
- In particular, the following restrictions apply
 - **Thermal limit:** Too high loading can lead to line sag (or rapid ageing in cables)
 - **Voltage drop:** For power quality and stability reasons, voltage magnitude at any bus in a network should not deviate by more than 10% from nominal value
 - **Transmission angle:** For stability reasons, the transmission angle should not exceed a certain maximum value, but a *steady-state stability margin* should be maintained

$$\text{steady-state stability margin} = \frac{P_{\max} - P_{\text{limit}}}{P_{\max}} \cdot 100\% \geq 30\%$$